
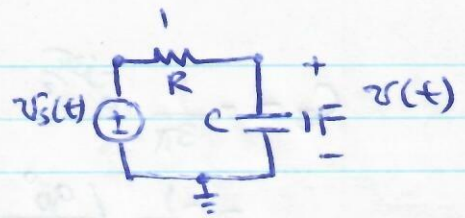


TOPIC 3

Ex2:

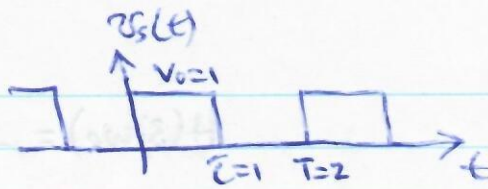

The transfer function of the filter

$$H(j\omega) = \frac{V(j\omega)}{V_s(j\omega)} = \frac{Z_C}{Z_C + Z_R} = \frac{1/j\omega C}{1/j\omega C + R}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

@ discrete points $\omega = n\omega_0$

$$H(jn\omega_0) = \frac{1}{1 + jn\omega_0 RC}$$

Thus,

$$v_n(t) = 2|C_n| |H(jn\omega_0)| \cos(n\omega_0 t + \angle C_n + \angle H(jn\omega_0))$$

and

$$v(t) = C_0 H(0) + \sum_{n=1}^{\infty} v_n(t)$$

now,

$$H(nj\omega_0) = \frac{1}{1 + jn\omega_0 RC} = \frac{1}{1 + jn \frac{2\pi}{T} \underbrace{RC}_{\frac{T}{2}}} = \frac{1}{1 + jn\pi}$$

for a pulse train

$$C_n = \frac{V_0 T}{T} \frac{\sin(n\pi \tau/T)}{(n\pi \tau/T)} e^{-jn\pi \tau/T}$$

$$= \frac{1}{2} \frac{\sin(n\pi/2)}{(n\pi/2)} e^{-jn\pi/2}$$

Evaluating The first few harmonics,

$$C_0 = \frac{1}{2}$$

$$H(0) = 1$$

$$C_1 = \frac{1}{\pi} e^{-j\pi/2}$$

$$H(j\omega_0) = \frac{1}{1 + j\pi} = 0.3033 \angle -72.3^\circ$$

$$C_2 = 0$$

$$C_3 = -\frac{1}{3\pi} e^{-j\frac{3\pi}{2}}$$

$$= -\frac{1}{3\pi} \angle 90^\circ$$

$$= \frac{1}{3\pi} \angle -90^\circ$$

$$C_4 = 0$$

$$C_5 = \frac{1}{5\pi} e^{-j\frac{\pi}{2}}$$

$$= \frac{1}{5\pi} \angle -90^\circ$$

$$C_6 = 0$$

$$C_7 = -\frac{1}{7\pi} e^{-j\frac{7\pi}{2}}$$

$$= -\frac{1}{7\pi} \angle 90^\circ$$

$$= \frac{1}{7\pi} \angle -90^\circ$$

$$H(3j\omega_0) = \frac{1}{1+j3\pi}$$

$$= 0.106 \angle -83.94^\circ$$

$$H(5j\omega_0) = \frac{1}{1+j5\pi}$$

$$= 0.0635 \angle -86.36^\circ$$

$$H(7j\omega_0) = \frac{1}{1+j7\pi}$$

$$= 0.04543 \angle -87.4^\circ$$

The source single sided FS is

$$v_s(t) = \frac{1}{2} + \frac{2}{\pi} \cos(\pi t - 90^\circ)$$

$$+ \frac{2}{3\pi} \cos(3\pi t - 90^\circ) + \frac{2}{5\pi} \cos(5\pi t - 90^\circ).$$

$$+ \frac{2}{7\pi} \cos(7\pi t - 90^\circ) + \dots$$

$$v(t) = \frac{1}{2} + 0.1931 \cos(\pi t - 162.34^\circ)$$

$$+ 0.0224 \cos(3\pi t - 173.94^\circ)$$

$$+ 0.0081 \cos(5\pi t - 176.36^\circ)$$

$$+ 0.0041 \cos(7\pi t - 177.4^\circ) + \dots$$

□

Ex4. 1V, 10 MHz, D-c = 50%

(a) 20 ns rise/fall time

$$\text{Duty-cycle (D)} = \frac{\bar{C}}{T}, \quad f_0 = \frac{1}{T}$$

for a trapezoidal waveform, first break frequency (f_1) is

$$f_1 = \frac{1}{\pi \tau} = \frac{1}{\pi (DT)} = \frac{f_0}{\pi D}$$

$$D = \frac{1}{2} \rightarrow f_1 = \frac{10 \times 10^6}{\pi \cdot \frac{1}{2}} = \boxed{6.37 \text{ MHz}}$$

Second break frequency (f_2),

$$f_2 = \frac{1}{\pi \tau_r} = \frac{10^9}{\pi \cdot 20} = \boxed{15.92 \text{ MHz}}$$


$$\text{Level}_{(10 \text{ MHz})} = 20 \log_{10}(10^6 \mu\text{V})$$

$$-20 \log_{10} \left(\frac{15.9 (\text{MHz})}{6.37 (\text{MHz})} \right)$$

$$-40 \log_{10} \left(\frac{110 (\text{MHz})}{15.9 (\text{MHz})} \right)$$

$$= 120 \text{ dB}\mu\text{V} - 7.95 \text{ dB}\mu\text{V} - 33.6 \text{ dB}\mu\text{V}$$
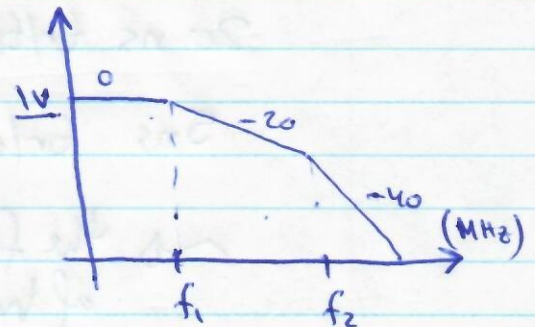
$$= \boxed{78.45 \text{ dB}\mu\text{V}}$$



(b) 5 ns rise/fall times.

$$\boxed{f_1 = 6.37 \text{ MHz}}$$

$$f_2 = \frac{10^9}{\pi \cdot 5} = \boxed{63.66 \text{ MHz}}$$

interpolate to find level @ 110 MHz


$$\text{Level}_{(110\text{MHz})} = 20 \log_{10}(10^6 \mu\text{V})$$

$$- 20 \log_{10}\left(\frac{63.66}{6.37}\right)$$

$$- 40 \log_{10}\left(\frac{110}{63.66}\right)$$

$$= 120 \text{ dB}\mu\text{V} - 19.99 - 9.5$$
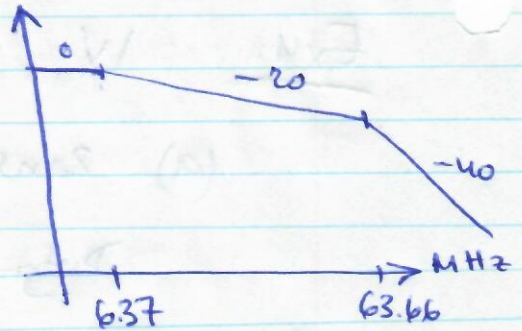
$$\text{Level}_{(110\text{MHz})} = \boxed{90.51 \text{ dB}\mu\text{V}}$$



• Comparing the Levels

$$20 \text{ ns tr/ef} \rightsquigarrow 78.45 \text{ dB}\mu\text{V}$$

$$5 \text{ ns tr/ef} \rightsquigarrow 90.51 \text{ dB}\mu\text{V}$$

\rightsquigarrow the faster rise time, the higher the level of harmonics at higher frequencies.

\rightsquigarrow try to slow the edges!

note: using exact values from the FS. coefficient we get

$$\begin{array}{lcl} 20 \text{ ns} & \rightsquigarrow & 73.8 \text{ dB}\mu\text{V} \\ 5 \text{ ns} & \rightsquigarrow & 90.4 \text{ dB}\mu\text{V} \end{array} \left. \vphantom{\begin{array}{lcl} 20 \text{ ns} \\ 5 \text{ ns} \end{array}} \right\} \begin{array}{l} \text{reasonably} \\ \text{close to} \\ \text{the} \\ \text{Bound.} \end{array}$$