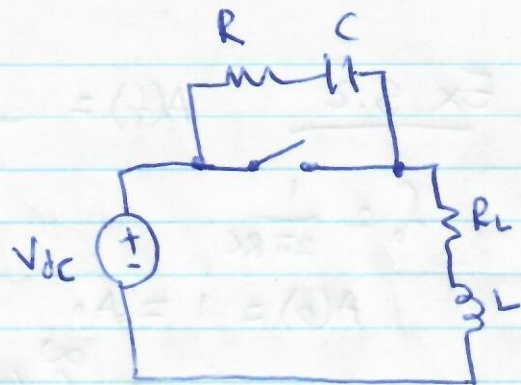


TOPIC 5EX 5.1

The value of R is chosen according to

$$\frac{V_{dc}}{I_{Amin}} < R < R_L$$

$$\frac{50}{0.25} < R < 500 \Rightarrow \boxed{200\Omega < R < 500\Omega}$$



To find C , two conditions should be satisfied

(a) to limit initial rate of rise of the available circuit voltage

$$\frac{V_{dc}}{CR_L} \leq E_{BV} = 10^8 \times 0.01 = 10^6$$

$$\Rightarrow C \geq \frac{V_{dc}}{R_L} \times 10^{-6} = 0.1 \mu F$$

(b) peak available circuit voltage must be below the voltage required to initiate a glow discharge

$$\frac{V_{dc}}{R_L} \sqrt{\frac{L}{C}} < 320 V$$

$$C \geq \left(\frac{1}{320} \frac{V_{dc}}{R_L} \right)^2 L$$

$$C \geq \left(\frac{1}{320} \times 0.1 \right)^2 (10^{-2}) = 976.6 \text{ pF} \\ = 0.0009766 \mu F$$

\Rightarrow choosing the largest of the two, we pick

$$\boxed{C = 0.1 \mu F}$$



Ex 5.2 $A(f) = \frac{f_0}{jf + f_0}$

$$f_0 = \frac{1}{2\pi RC}$$

$$A(0) = 1 = A_0$$

Now, $B = \frac{1}{\pi} \int_0^\infty \left(\left| \frac{f_0}{jf + f_0} \right|^2 \right) df$

$$= f_0^2 \int_0^\infty \left(\frac{1}{\sqrt{f^2 + f_0^2}} \right)^2 df$$

$$= f_0^2 \int_0^\infty \left((f^2 + f_0^2)^{-1} \right) df$$

integration by substitution

let $f = f_0 \tan \theta$ and $df = f_0 \sec^2 \theta d\theta$

$$\Rightarrow B = f_0^2 \int_0^{\pi/2} \frac{1}{f_0^2 \tan^2 \theta + f_0^2} \cdot f_0 \sec^2 \theta d\theta$$

$$= f_0 \int_0^{\pi/2} \frac{1}{\tan^2 \theta + 1} \cdot \sec^2 \theta d\theta$$

recall that $\tan^2 \theta + 1 = \sec^2 \theta$

$$\Rightarrow B = f_0 \int_0^{\pi/2} d\theta$$

$$B = \frac{\pi}{2} f_0$$

i.e. $1.57 \times \frac{f_0}{30 \text{ dB BW}}$

\square

Ex: 5.3

@ the input of the TV, the 300Ω T-line, generates a thermal noise voltage of

$$\left(\begin{array}{l} \text{open circuit} \\ \text{thermal} \\ \text{noise} \\ \text{voltage} \end{array} \right) V_{t_0} = \sqrt{4kTB} = \sqrt{4 \times 1.38 \times 10^{-23} \times 290 \times 300 \times 4 \times 10^6}$$


$$= 4.3829 \mu\text{V}$$

$$V_{t-TV} = \frac{1}{2} V_{t_0}$$

$$= 2.1915 \mu\text{V}$$

$$= 6.815 \text{ dB}\mu\text{V}$$

$$= -53.2 \text{ dBmV}$$

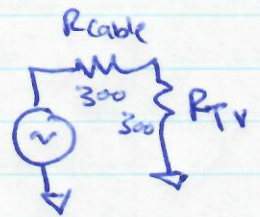

All impedances
are referred
to 300Ω

The TV will add 14 dB of noise (Because of its 14 dB NF)

then, $V_{in-TV-noise} = -53.2 + 14$


$$= -39.2 \text{ dBmV}$$

Since we need 40 dB SNR , then signal level @ TV input should be

$$V_{sig}|_{\text{dB}} = \text{SNR}|_{\text{dB}} + V_{in-TV-noise}$$

$$= 40 - 39.2 = 0.8 \text{ dBmV}$$

$$V_{sig-ant}|_{\text{dB}} = 6 + 0.8 = 6.8 \text{ dBmV}$$

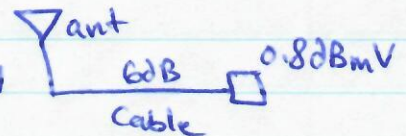

$$V_{sig-ant}|_r = 2.19 \text{ mV}$$

