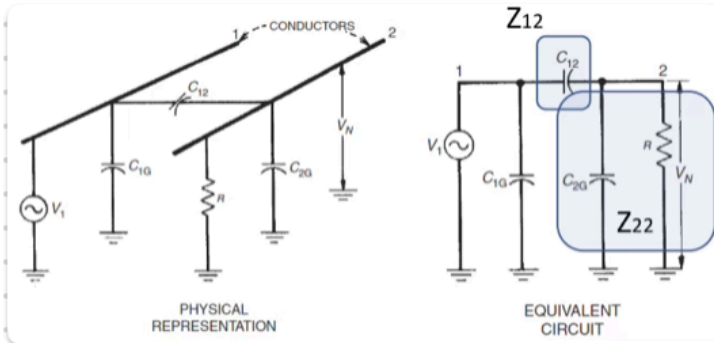


Q1

Q1 [5 pts]: Show the detailed steps to get (derive) the equation shown in T6 slide 3 for  $V_N$  from the equivalent circuit model shown on the same slide.



Derive,  $V_N = j\omega R C_{12} V_1$

1. Rewrite  $Z_{22}$  in terms of  $C_{20}$  and  $R$  impedance,

$$Z_{12} = \frac{1}{j\omega C_{12}} \quad Z_{20} = \frac{1}{j\omega C_{20}}$$

$$Z_{22} = \frac{1}{j\omega C_{20} + \frac{1}{R}} = \frac{R}{j\omega C_{20} R + 1}$$

2. Treat  $Z_{12}$  and  $Z_{22}$  as a voltage divider to solve for  $V_N$ ,

$$V_N = \left( \frac{Z_{22}}{Z_{12} + Z_{22}} \right) V_1 = \frac{\frac{R}{j\omega C_{20} R + 1}}{\frac{R}{j\omega C_{20} R + 1} + \frac{1}{j\omega C_{12}}} V_1 = \frac{j\omega C_{12} R}{j\omega C_{12} R + j\omega C_{20} R + 1} V_1$$

$$V_N = \frac{j\omega C_{12} R}{j\omega R (C_{12} + C_{20}) + 1} V_1$$

3. Assume  $R \ll j\omega (C_{12} + C_{20})$ ,

$$V_N = \frac{j\omega C_{12} R}{j\omega R (C_{12} + C_{20}) + 1} V_1 = \frac{j\omega C_{12} R}{1} V_1 = j\omega R C_{12} V_1$$

Q2

$$V(0,t) = \frac{Z_c}{R_s + Z_c} V_s(t) = \frac{55}{11 + 55} (5) = \frac{275}{66} = 4.167 \text{ V}$$

$$I(0,t) = \frac{V_s(t)}{R_s + Z_c} = \frac{5}{80} = \frac{1}{16} \text{ A} = 62.5 \text{ mA}$$

$$a) \quad \Gamma_s = \frac{R_s - Z_c}{R_s + Z_c} = \frac{11 - 55}{11 + 55} = \frac{-44}{66} = -\frac{2}{3}$$

$$\Gamma_L = \frac{R_L - Z_c}{R_L + Z_c} = \frac{275 - 55}{275 + 55} = \frac{220}{330} = \frac{2}{3}$$

$$b) \quad @ 1 \mu s, \quad V_{1L} = V_{0s} + V_{0s} \Gamma_L = 4.167 + (4.167) \left( \frac{2}{3} \right) = 4.167 + 2.78 \text{ V} = 6.947 \text{ V}$$

$$V_{1R} = 2.78 \text{ V}$$

$$@ 2 \mu s, \quad V_{1s} = 6.947 + \left( \frac{2}{3} \right) (2.78) = 5.0834 \text{ V}$$

$$@ 3 \mu s, \quad V_{2L} = V_{1s} + (V_{1R}) (\Gamma_s) (\Gamma_L) = 5.0834 - 1.236 = 3.848 \text{ V}$$

$$V_{2R} = -1.236 \text{ V}$$

$$@ 4 \mu s, \quad V_{2s} = V_{2L} + (V_{2R}) (\Gamma_s) = 3.848 + (-1.236) \left( -\frac{2}{3} \right) = 4.672 \text{ V}$$

$$@ 5 \mu s, \quad V_{3L} = V_{2s} + (V_{2R}) (\Gamma_s) (\Gamma_L) = 4.672 + 0.549 = 5.221 \text{ V}$$

$$V_{3R} = 0.549 \text{ V}$$

$$@ 6 \mu s, \quad V_{3s} = V_{3L} + (V_{3R}) (\Gamma_s) = 5.221 - 0.366 = 4.855 \text{ V}$$

$$@ 7 \mu s, \quad V_{4L} = V_{3s} + (V_{3R}) (\Gamma_s) (\Gamma_L) = 4.855 - 0.244 = 4.611 \text{ V}$$


$$V_{4R} = -0.244 \text{ V}$$

$$@ 8 \mu s, \quad V_{4s} = V_{4L} + (V_{4R}) (\Gamma_s) = 4.611 + 0.162 = 4.774 \text{ V}$$

$$@ 9 \mu s, \quad V_{5L} = V_{4s} + (V_{4R}) (\Gamma_s) (\Gamma_L) = 4.774 + 0.1084 = 4.882 \text{ V}$$

$$V_{5R} = 0.1084 \text{ V}$$
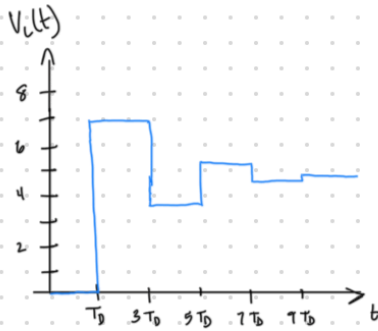
$$@ 10 \mu s, \quad V_{5s} = V_{5L} + (V_{5R}) (\Gamma_s) = 4.882 - 0.072 = 4.810 \text{ V}$$



$$c) \quad V_L(l, t) = \frac{Z_c}{R_s + Z_c} (1 + \Gamma_L) \left[ V_s(t - T_D) + \Gamma_S \Gamma_L V_s(t - 3T_D) + (\Gamma_S \Gamma_L)^2 V_s(t - 5T_D) + (\Gamma_S \Gamma_L)^3 V_s(t - 7T_D) + (\Gamma_S \Gamma_L)^4 V_s(t - 9T_D) \right]$$

$$\frac{Z_c}{R_s + Z_c} (1 + \Gamma_L) = \frac{25}{11 + 25} \left( 1 + \frac{2}{3} \right) = \left( \frac{5}{6} \right) \left( \frac{5}{3} \right) = \frac{25}{18}$$


$$@ 1\mu s, \quad V_L(l, T_D) = \frac{25}{18} (5) = (1.389)(5) = 6.94 \text{ V}$$

$$@ 3\mu s, \quad V_L(l, 3T_D) = \frac{25}{18} \left( 5 + \left(-\frac{4}{3}\right)(5) \right) = \frac{25}{18} \left( 5 + (-0.7)(5) \right) = \frac{25}{18} (5 - 2.7) = 3.86 \text{ V}$$

$$@ 5\mu s, \quad V_L(l, 5T_D) = \frac{25}{18} \left( 5 + \left(-\frac{4}{3}\right)(5) + \left(\frac{4}{3}\right)^2(5) \right) = \frac{25}{18} \left( 5 + (-0.77)(5) + (0.1775)(5) \right) = \frac{25}{18} (2.7 + 0.79) = \frac{25}{18} (3.77) = 5.23 \text{ V}$$

$$@ 7\mu s, \quad V_L(l, 7T_D) = \frac{25}{18} \left( 5 + \left(\frac{4}{3}\right)(5) + \left(-\frac{4}{3}\right)^2(5) + \left(-\frac{4}{3}\right)^3(5) \right) = \frac{25}{18} \left( 3.77 + (5) \left(-\frac{4}{3}\right)^3 \right) = \frac{25}{18} (3.77 - 0.49) = \frac{25}{18} (3.32) = 4.63 \text{ V}$$

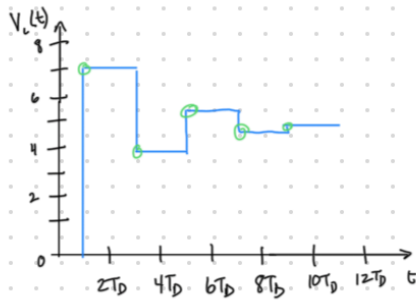
$$@ 9\mu s, \quad V_L(l, 9T_D) = \frac{25}{18} \left( 5 + \left(\frac{4}{3}\right)(5) + \left(-\frac{4}{3}\right)^2(5) + \left(-\frac{4}{3}\right)^3(5) + \left(\frac{4}{3}\right)^4(5) \right) = \frac{25}{18} \left( 3.32 + (5) \left(-\frac{4}{3}\right)^4 \right) = \frac{25}{18} (3.32 + 0.195) = \frac{25}{18} (3.525) = 4.89 \text{ V}$$





- e) After the line's  $T_D$ , the  $V_L(t)$  saturated because the source impedance matched the transmission line's characteristic impedance. There was no ringing on the load. There was a small ring on  $V_{in}(t)$ , as the reflected load voltage caused  $V_{in}(t)$  to match  $V_S(t)$  on  $2T_D$ .

f) Similar to e), the load voltage immediately saturated to the maximum  $V_L$  with no ringing, at  $T_D$ . Unlike e),  $V_L(t)$  settled to its maximum value at time 0.

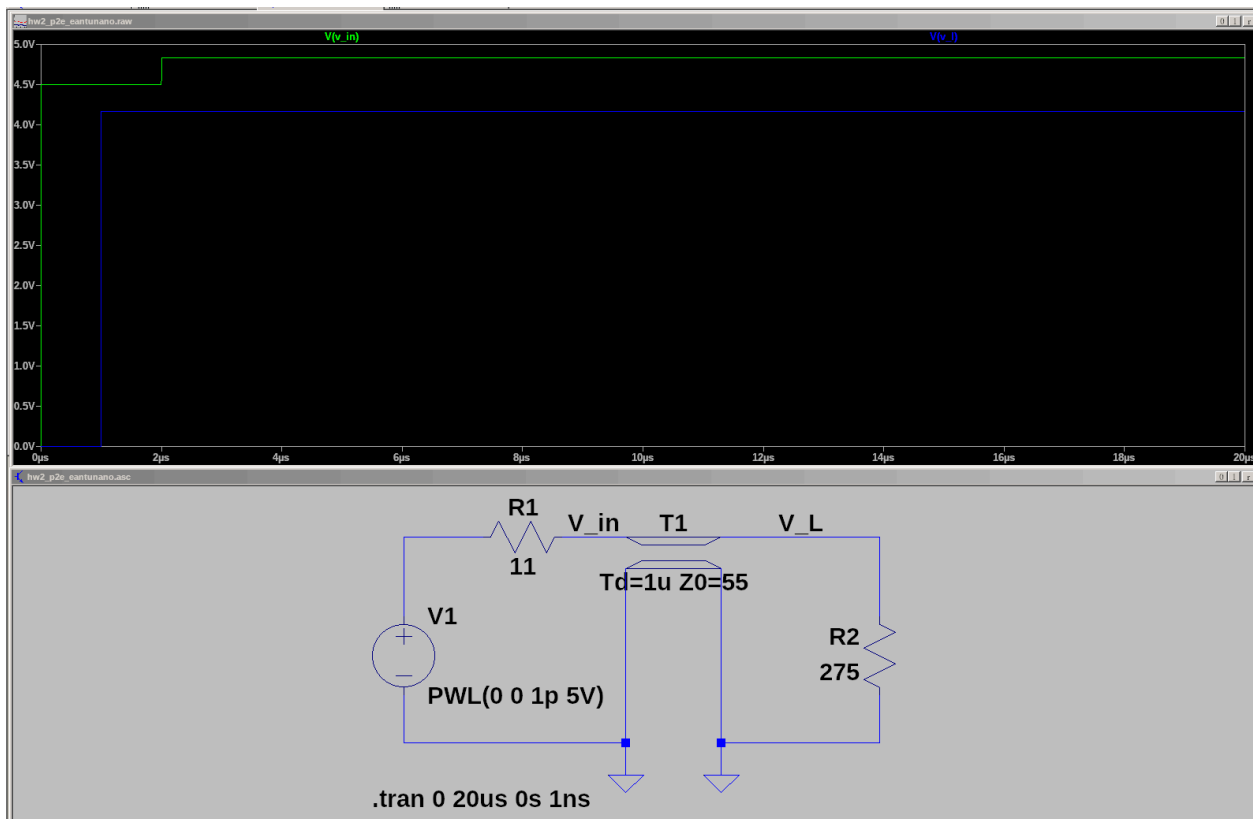g) In general, the voltage rating for the receiver should be set to the value of  $V_L$  at time  $T_D$ , the time step with the worst-case ringing. Use the following formula for the exact voltage rating,  $V_L(l, T_D) = \frac{Z_0}{R_S + Z_0} (1 + \Gamma_L) (V_S(t - T_D))$



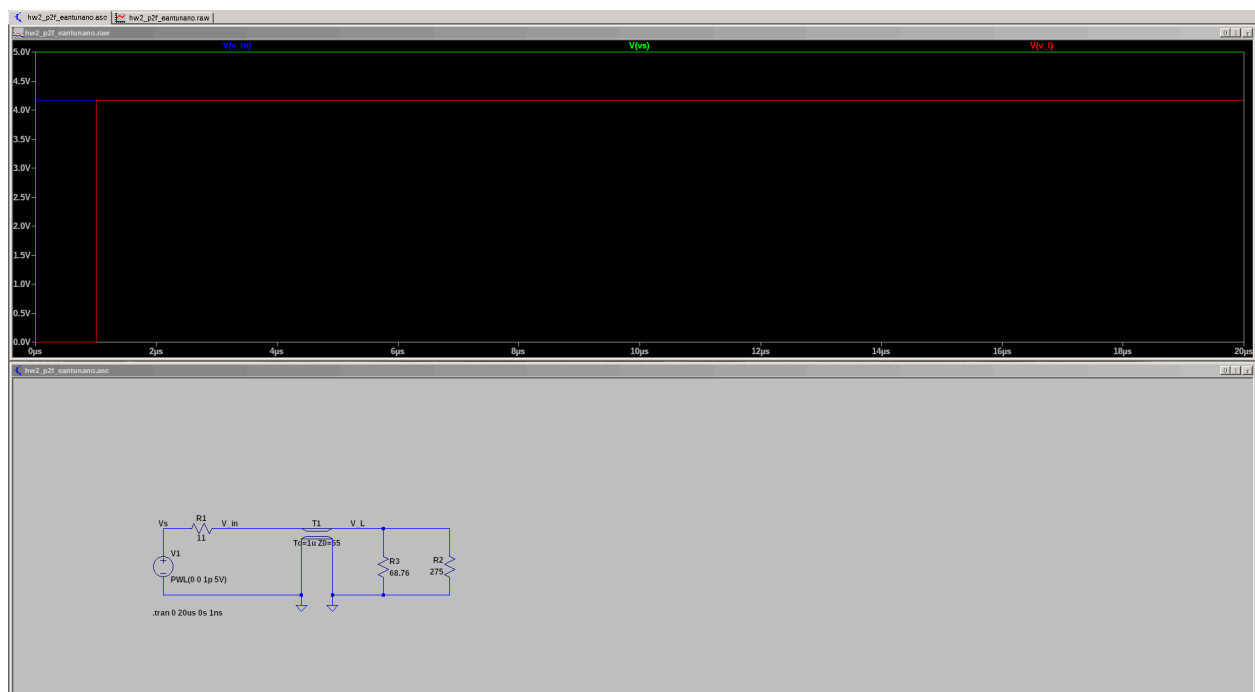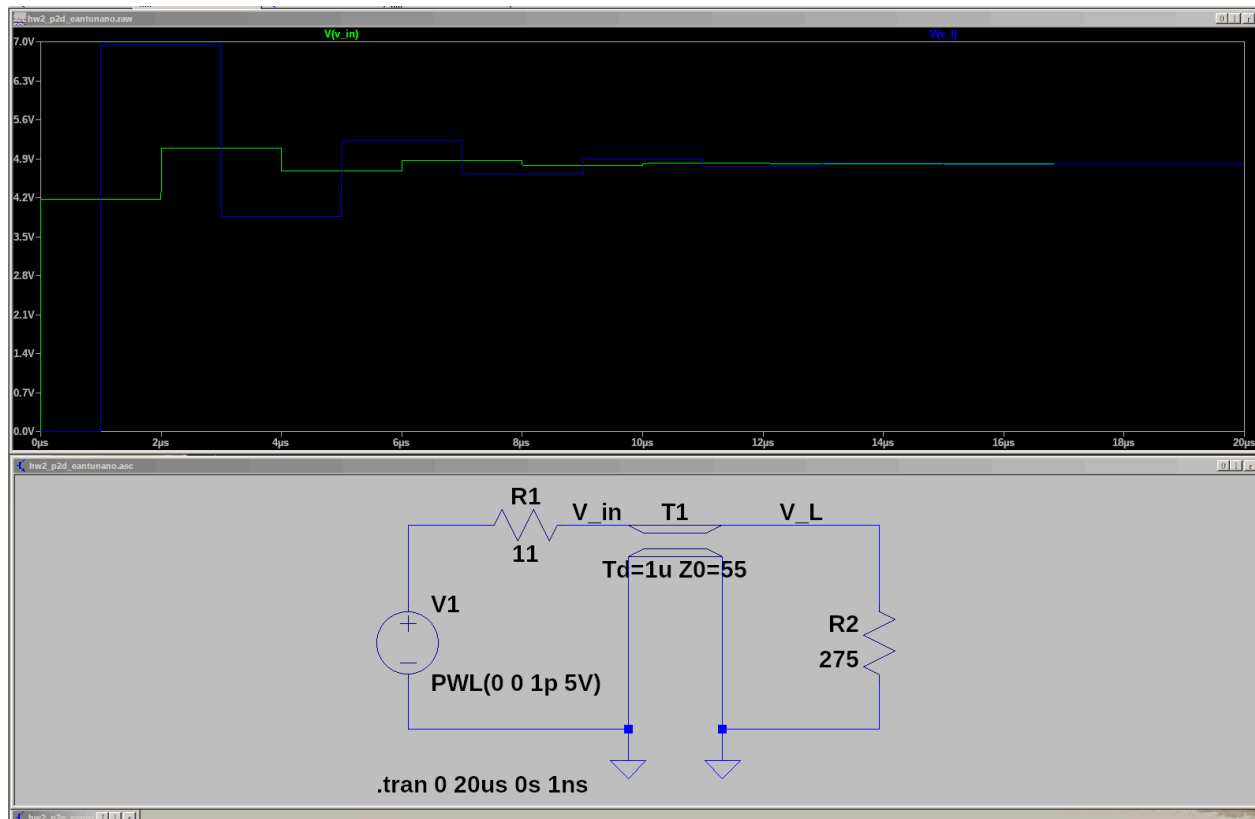

### Q3

a)  $\lambda = \frac{V_d}{f} = \frac{3 \text{ EB}}{5 \text{ EB}} = 0.6 \text{ EB} = 60$

$f\left(\frac{L}{V}\right) = 5 \text{ EB} \left(\frac{78}{60}\right) = \boxed{1.5}$

b)  $\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$ ;  $Z_0 = Z_L$  both signs used interchangeably depending on textbook

$\Gamma_s = \frac{30 - j30 - 50}{30 - j30 + 50} = \frac{-20 - j30}{80 - j30} \rightarrow \frac{-20 - j30}{80 - j30} \left( \frac{80 + j30}{80 + j30} \right) = \frac{-2100 - j2100 - j2400 + 900}{4700 + 900} = \frac{-1200 - j3000}{5600} =$

$-0.207 - j0.517 \xrightarrow{\text{std 2 polar form}} r = \sqrt{(-0.207)^2 + (-0.517)^2} = 0.557$   
 $\theta = \text{atan}\left(\frac{-0.517}{-0.207}\right) = \text{atan}\left(\frac{0.517}{0.207}\right) + \pi = 1.170$  (accounts for numerator & denominator both being negative (2<sup>nd</sup> quadrant))  
 Euler Format  $\rightarrow \boxed{0.557 e^{j1.17}}$

$\Gamma_o = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - j500 - 50}{100 - j500 + 50} = \frac{50 - j500}{150 - j500} = \frac{50 - j500}{150 - j500} \left( \frac{150 + j500}{150 + j500} \right) = \frac{37500 + j75000 - j125000 + 250000}{62500 + 250000} = \frac{287500 - j50000}{512500} =$

$= 0.72 - j0.16 \xrightarrow{\text{std 2 polar form}} r = \sqrt{(0.72)^2 + (0.16)^2} = 0.734$   
 $\theta = \text{atan}\left(\frac{-0.16}{0.72}\right) = \text{atan}\left(\frac{-0.16}{0.72}\right) = -0.172$  Euler Format  $\rightarrow \boxed{0.734 e^{-j0.172}}$

$$c) \quad \beta = \omega \sqrt{LC} = \frac{\omega}{v_p} = \frac{2\pi}{\lambda}$$

$$\beta = \frac{2\pi}{60} = \frac{\pi}{30}$$

$$Z_{in}(-l) = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

$$Z_{in}(-78) = 50 \left( \frac{200 - j500 + j(50)(\tan(\frac{\pi}{30} \cdot 78))}{50 + j(200 - j500) \tan(\frac{\pi}{30} \cdot 78)} \right)$$

$$= 50 \left( \frac{200 - j500 + j \tan(\frac{13\pi}{5})(50)}{50 + j(200 - j500) \tan(\frac{13\pi}{5})} \right)$$

$$= 50 \left( \frac{200 - j500 + j(-3.078)50}{50 + j(200 - j500)(-3.078)} \right)$$

$$= 50 \left( \frac{200 - j500 - j153.88}{50 - j615.5 - 1538.84} \right)$$

$$= 50 \left( \frac{200 - j653.88}{-1488.84 - j615.5} \right)$$

$$= 50 \left( \frac{200 - j653.88}{-1488.84 - j615.5} \right) \left( \frac{-1488 + j615.5}{-1488 + j615.5} \right)$$

$$= 50 \left( \frac{-297600 + j972973.44 + j123100 + 402463.14}{2214144 + 378840.25} \right)$$

$$= 50 \left( \frac{104863.14 + j1096073.44}{2592984.55} \right)$$

$$\boxed{Z_{in} = 2.02 + j21.14}$$



$$d) V_{in} = V_s \left( \frac{Z_{in}}{Z_{in} + Z_s} \right)$$

$$\begin{aligned} V_{in} &= V_s \left( \frac{Z_{in}}{Z_{in} + Z_s} \right) \\ &= 50 \angle 0^\circ \left( \frac{2.02 + j21.14}{2.02 + j21.14 + 20 - j30} \right) \\ &= 50 \angle 0^\circ \left( \frac{2.02 + j21.14}{22.02 - j8.86} \right) \\ &= 50 \angle 0^\circ \left( \frac{21.24 \angle 89.54^\circ}{23.74 \angle -21.72^\circ} \right) \end{aligned}$$

$$\begin{aligned} r_n &= \sqrt{2.02^2 + 21.14^2} = 21.24 \\ \theta_n &= \tan^{-1} \left( \frac{21.14}{2.02} \right) = 89.54^\circ \\ r_d &= \sqrt{22.02^2 + 8.86^2} = 23.74 \\ \theta_d &= \tan^{-1} \left( \frac{-8.86}{22.02} \right) = -21.72^\circ \end{aligned}$$

$$= 50 \angle 0^\circ (0.895 \angle 106.46^\circ)$$

$$V_{in} = 44.75 \angle 106.46^\circ$$

$$V_{in} = 44.75 e^{j1.86}$$

$$\frac{106.46}{180} \pi = 1.86 \text{ rad}$$

$$V_{in} = 44.75 (\cos(1.86) + j \sin(1.86)) \xrightarrow{\text{time-domain}} r(\cos(\omega t + \phi) + j \sin(\omega t + \phi))$$

$$V_{in}(t) = 44.75 (\cos(10\pi 56 t + 1.86) + j \sin(10\pi 56 t + 1.86))$$

Lec 4, Slide 34

$$V(z) = V^+(e^{-j\beta z} + \Gamma_0 e^{j\beta z})$$

$$V_L = V_{in} e^{-j\beta L} (1 + \Gamma_L)$$

$$\begin{aligned} &= 44.75 \angle 106.46^\circ e^{-j(72)(\frac{\pi}{360})} (1 + 0.92 - j0.16) \\ &= 44.75 \angle 106.46^\circ e^{-j9.17^\circ} (1.12 + j0.16) \end{aligned}$$

$$360 = 6.2832 \text{ rad}$$

$$= 44.75 \angle 106.46^\circ e^{-j9.17^\circ} 1.73 \angle 4.76^\circ$$

$$= 44.75 \angle 106.46^\circ e^{-j9.17^\circ} 1.73 \angle 4.76^\circ$$

$$= 86.39 \angle 111.55^\circ e^{-j106.79^\circ}$$

$$= 86.39 \angle 111.55^\circ 1 \angle -106.79^\circ$$

$$= 86.39 \angle 4.76^\circ$$

$$V_L = 86.39 e^{j0.083}$$

$$\xrightarrow{\text{time-domain}} r(\cos(\omega t + \phi) + j \sin(\omega t + \phi))$$

$$V_L(t) = 86.39 (\cos(10\pi 56 t + 0.083) + j \sin(10\pi 56 t + 0.083))$$

$$\begin{aligned}
 e) \quad P_{av} &= \frac{1}{2} \operatorname{Re} \{ V I^* \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ \frac{(86.39 \angle 0.08912)^2}{200 - j500} \right\} \\
 &= \frac{1957.66 e^{j0.1786}}{538.52 \angle -68.2} \quad \frac{3.54 \cdot 180}{\pi} = 202.827 \\
 &= \frac{1957.66 \angle 271.703}{538.52 \angle -68.2} \\
 &= \frac{1}{2} \operatorname{Re} \{ 3.64 \angle 271.703 \} \\
 &= \frac{1}{2} \cdot r \cos(\theta) \\
 &= \frac{1}{2} (3.64) \cos(271.703) \\
 &= \frac{1}{2} (3.95) \\
 \boxed{P_{av} = 1.475 \text{ W}}
 \end{aligned}$$

$$\begin{aligned}
 f) \quad VSWR &= \left| \frac{V_{max}}{V_{min}} \right| = \left| \frac{I_{max}}{I_{min}} \right| = \frac{1 + |\Gamma_o|}{1 - |\Gamma_o|} \\
 &= \frac{1 + |0.934 e^{j0.172}|}{1 - |0.934 e^{j0.172}|} \\
 &= \frac{1 + 0.934}{1 - 0.934} \\
 \boxed{VSWR = 29.3}
 \end{aligned}$$

$$T_D = \left(\frac{1}{f}\right)(\lambda) = \left(\frac{1}{5\text{MHz}}\right)(1.3) = 260\text{ns}$$

Negative imaginary number indicates capacitor  $Z = \left(\frac{1}{j\omega C}\right)$   
 Positive imaginary indicates inductor  $Z = j\omega L$

$$Z_S = \frac{1}{j\omega C_S}$$

$$C_S = \frac{1}{j\omega Z_S}$$

$$= \frac{1}{j(2\pi)(5E6)(-j30)}$$

$$= \frac{1}{2\pi(5E6)(30)}$$

$$C_S = 1\mu\text{F}$$

$$C_L = \frac{1}{2\pi(5E6)(500)}$$


$$= \frac{1}{2\pi(5)(5)(10^6)(10^2)}$$

$$= \frac{1}{(10^6)(10^2)(10^2)(1.571)}$$


$$= 0.64 \times 10^{-10}$$

$$C_L = 64\text{pF}$$


## Impedance

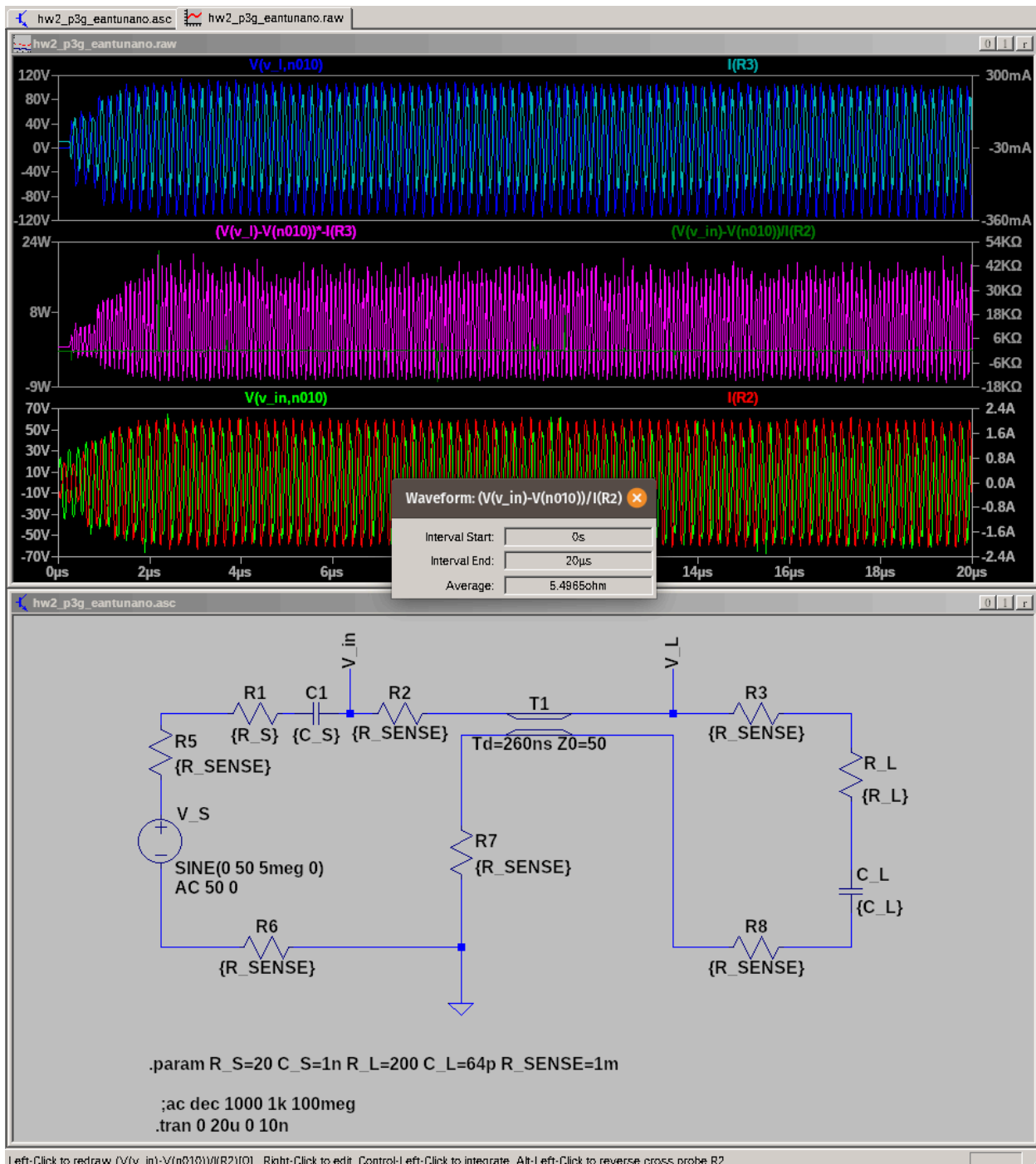


## Vin Value

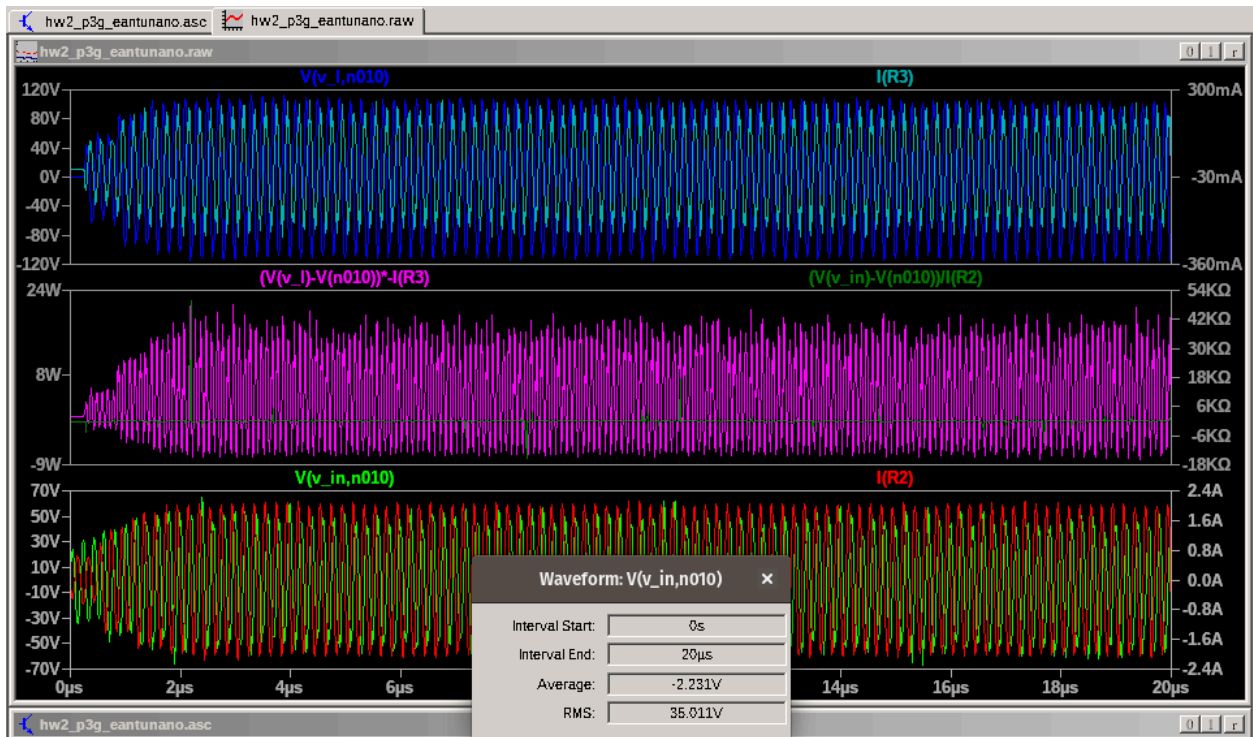



V\_L voltage

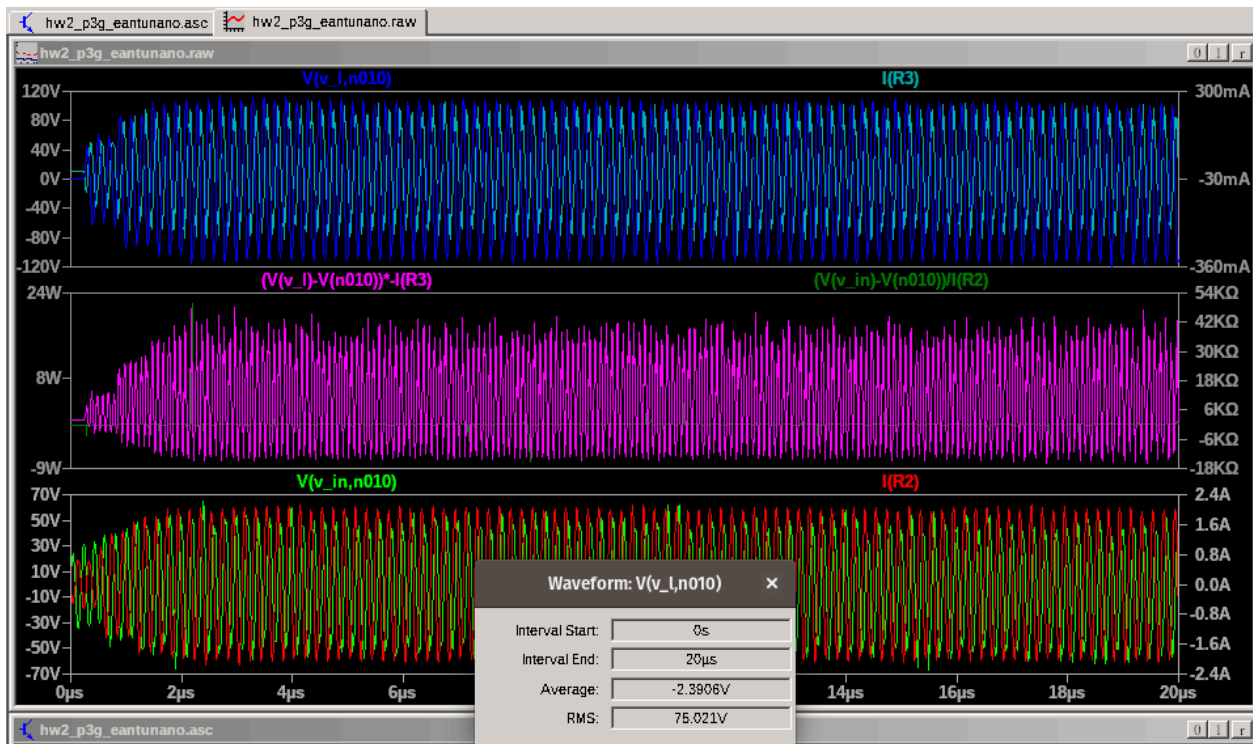

Average Power

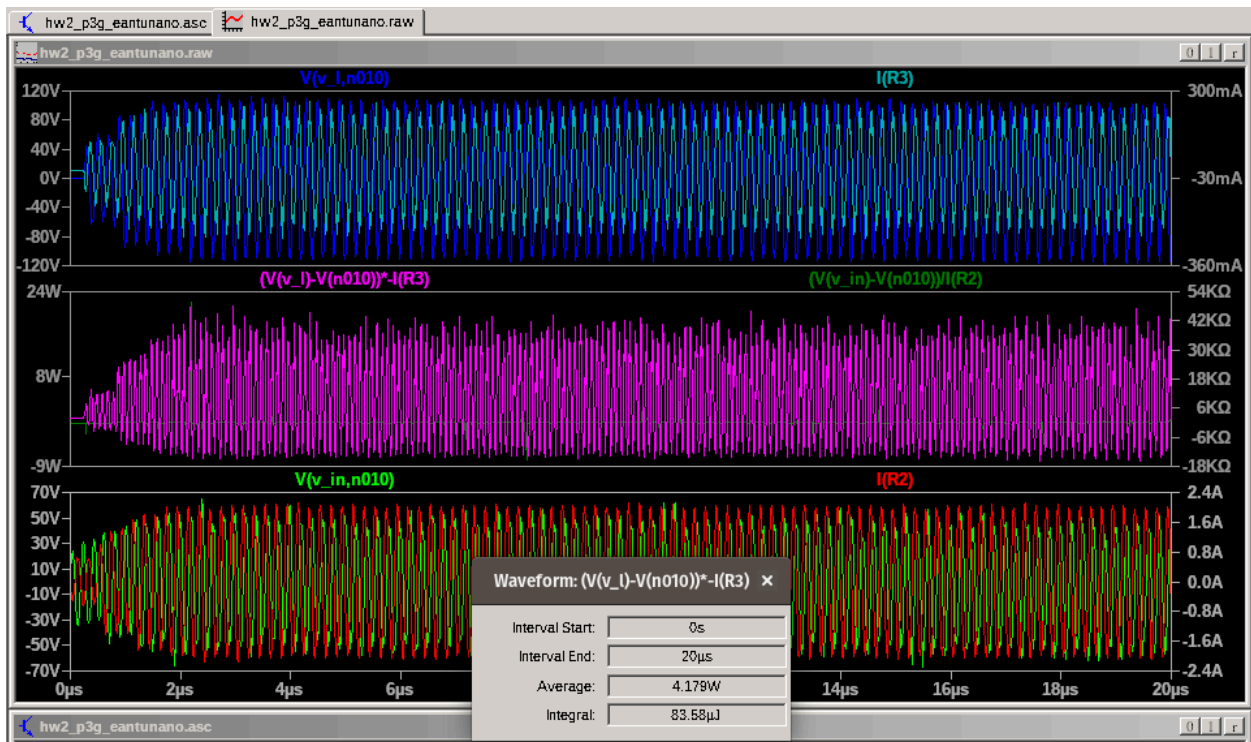

# Q4

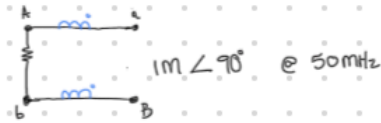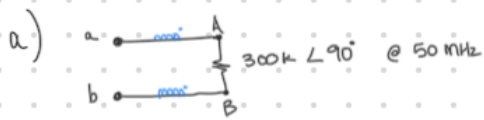

$$\hat{Z}_1 = \frac{\hat{V}_1}{\hat{I}_1} = \frac{j\omega(L\hat{I}_1 + m\hat{I}_2)}{\hat{I}_1}$$

Considering  $\hat{I}_1 = \hat{I}_c$  and  $\hat{I}_2 = \hat{I}_c$  then,

$$\hat{Z}_{cm} = j\omega(L+m) + j\omega(L+m)$$

$$\begin{aligned} 300k \angle 90^\circ &= j(2\pi f)(L+m) + j(2\pi f)(L+m) \\ &= j2(\pi \times 8)(L+m) \\ 300k(\cos(90^\circ) + j\sin(90^\circ)) &= j2\pi \times 8(L+m) \\ 300k(j1) &= j2\pi \times 8(L+m) \\ \frac{j300k}{j2\pi \times 8} &= L+m \end{aligned}$$

$$L+m = 0.478 \text{ mH}$$

$$m = 0.478 \text{ mH} - L$$

$$L = 0.478 \text{ mH} + L = 1.592 \text{ mH}$$

$$2L = 2.07 \text{ mH}$$

$$L = 1.035 \text{ mH}$$

$$m = 0.478 \text{ mH} - 1.035 \text{ mH}$$

$$m = -0.557 \text{ mH}$$

$$\hat{Z}_{dm} = j\omega(L-m) + j\omega(L-m)$$


$$\begin{aligned} 1m \angle 90^\circ &= j(2\pi f)(L-m) + j2\pi f(L-m) \\ &= j2\pi(50)[ \\ &= j\pi \times 8(L-m) + j\pi \times 7(L-m) \\ j1000 &= j2\pi \times 8(L-m) \end{aligned}$$

$$\frac{j1000}{j2\pi \times 8} = L-m$$

$$L-m = 1.592 \text{ mH}$$

Top Graph: Differential Impedance

## Bottom Graph: Common Mode Impedance

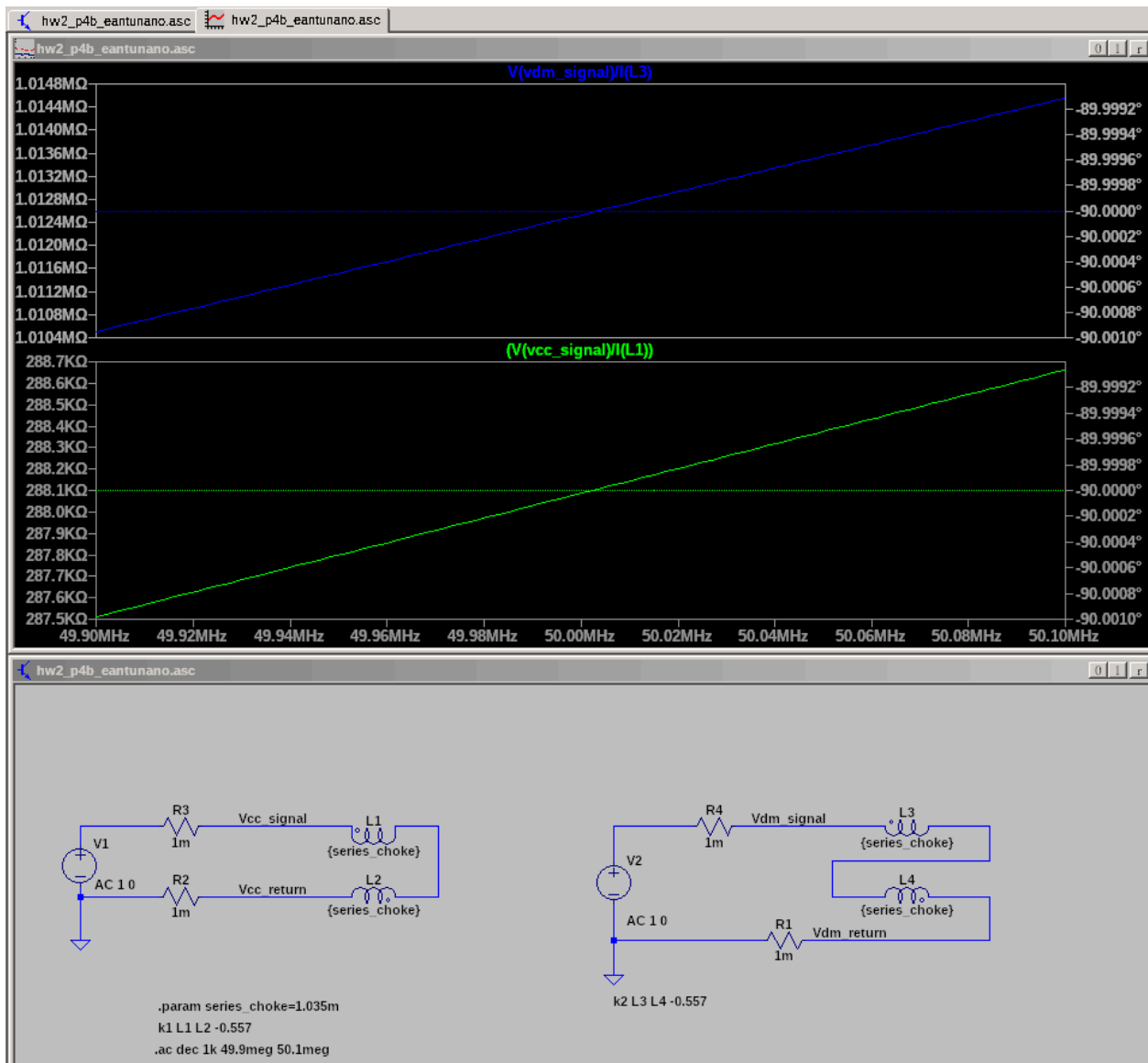



Q5

a)


Assuming room temperature operation,

$k$  = Boltzmann's constant  $(1.38 \times 10^{-23} \text{ J/K})$

$T$  = temp. in kelvins

$B$  = bandwidth in Hz

$R$  = resistance in ohms

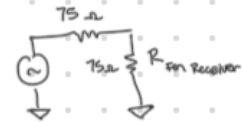

$$V_{E_o} = \sqrt{4kTRB}$$

$$= \sqrt{4(1.38 \times 10^{-23})(290)(75)(50 \times 10^3)}$$

$$= 0.245 \mu V$$

$$V_{E_{-fm \text{ receiver}}} = \frac{1}{2}(0.245)$$

$$= 0.1225 \mu V \quad \mu V \text{ to mV} \rightarrow 0.0001225 mV$$

$$= 20 \log_{10}(0.1225) = 20 \log_{10}(0.0001225)$$

$$= -18.24 dB\mu V = -78.24 dBmV$$

The FM Receiver will add 8 dB of noise then,

$$V_{in-FM} = -78.24 + 8$$

$$V_{in-FM} = -70.24 dBmV$$

18 dB SNR, then signal level @ FM Receiver input should be,


$$V_{sig1dB} = SNR_{1dB} + V_{in-FM}$$

$$= 18 - 70.24$$

$$= -52.24 dBmV$$

$$V_{sig-ant1dB} = 6 - 52.24$$

$$= -46.24 dBmV$$

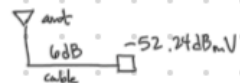

$$V_{sig-ant1dB} = 10^{\left(\frac{-46.24}{20}\right)} = 0.00487 mV$$

b) FM receiver does not require as clean or noiseless signal compared to a TV. So, the input voltage can have a lower SNR, thus leading to a lower input signal than a TV, which has a much larger SNR.