

Q1

EE P 592 / EE 579A


# Electromagnetic Compatibility

HW3

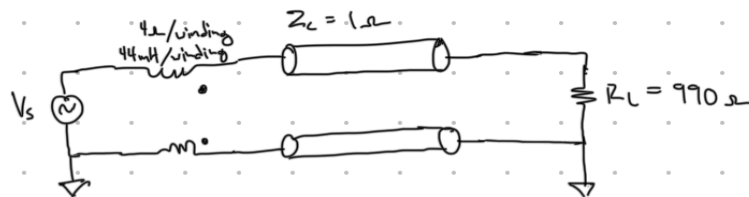**Q1 [8 pts]:** A common-mode choke is placed in series with a transmission line that connects a low impedance source to a  $900\Omega$  load. The transmission line conductors each have a  $1\Omega$  resistance. Each winding of the common-mode choke has an inductance of  $0.044\text{H}$  and a resistance of  $4\Omega$ .

- Above what frequency will the choke have a negligible effect on the signal transmission?
- How much attenuation (in dB) does the choke provide to a ground differential noise voltage at  $60\text{Hz}$ ,  $180\text{Hz}$  and  $300\text{Hz}$ .

EMC - T.7 - Sharawi, pdf  
Topic: Grounding



Assume identical windings so that  $L_1 = L_2 = M$  } slide 22  
Also,  $Z_c \ll R_L$  so  $Z_c$  can be ignored

- For signal frequencies greater than  $\omega = 5R_{cz}/L_z$ , virtually all the current will go via the second conductor and not the ground plane.

Since  $L_1 = L_2 = M$  the following formula  $V_s = j\omega(L_1 + L_2)I_s - 2j\omega MI_s + (R_{cz} + R_L)I_s$   
simplifies to  $I_s = \frac{V_s}{(R_{cz} + R_L)}$

Then since  $R_{cz} \ll R_L$  it simplifies to  $I_s = V_s/R_L$ ,  
again only when signal frequency is greater than  $\omega = 5R_{cz}/L_z$

Question:

- Does the transmission line resistance factor into the common mode choke frequency formula?

$$\omega = 5R_{cz}/L_z$$

$$2\pi f = 5R_{cz}/L_z$$

$$f = \frac{5R_{cz}}{2\pi L_z} = \frac{5(4\Omega + 1\Omega)}{2\pi(44\text{mH})} = \frac{5(5)}{2\pi(0.088)} = 90.43\text{ Hz}$$

b) Lecture 7, slide 24  $V_N = \frac{V_L R_{C2}/L}{j\omega + R_{C2}/L}$

$$A_{dB} = 20 \log_{10} \left( \left| \frac{V_N(f)}{V_G(f)} \right| \right) = 20 \log_{10} \left| \frac{\left( \frac{V_L R_{C2}/L}{j\omega + R_{C2}/L} \right)}{V_G} \right| = 20 \log_{10} \left| \left( \frac{R_{C2}}{j\omega L + R_{C2}} \right) \right|$$

$$A_{dB}(60\text{Hz}) = 20 \log_{10} \left( \frac{(4+1)}{j(2\pi(60)(0.044)) + (4+1)} \right) = 20 \log_{10} \left| \frac{5}{5 + j16.51} \right| = 20 \log_{10} \left( \frac{5}{17.33} \right) = -10.80 \text{ dB}$$

$$A_{dB}(186\text{Hz}) = 20 \log_{10} \left( \frac{(4+1)}{j(2\pi(186)(0.044)) + (4+1)} \right) = 20 \log_{10} \left| \frac{5}{5 + j49.76} \right| = 20 \log_{10} \left( \frac{5}{49.96} \right) = -19.91 \text{ dB}$$

$$A_{dB}(300\text{Hz}) = 20 \log_{10} \left( \frac{(4+1)}{j(2\pi(300)(0.044)) + (4+1)} \right) = 20 \log_{10} \left| \frac{5}{5 + j82.74} \right| = 20 \log_{10} \left( \frac{5}{83.08} \right) = -24.4 \text{ dB}$$

## Q2

**Q2 [10 pts]:** For the Differential amplifier shown in Figure 1,  $R_1$  and  $R_2$  are 1% resistors with values of  $4.7 \text{ k}\Omega$  and  $270 \text{ k}\Omega$ , respectively.

- Calculate the Differential mode (DM) input impedance.
- What is the differential mode gain?
- Calculate the common-mode (CM) input impedance?
- What is the common mode gain?
- What will be the value of the CMRR?

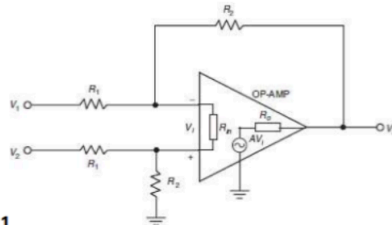


Figure 1

EMC-T8-Shorasi.pdf  
Topic: Filtering and balancing

S10; if the load resistors have tolerance of  $\pm x\%$ , the max variation (unbalance) will be  $2x\%$  because path 1 resistance can be  $R + \Delta R$  (tolerance) versus path 2  $R - \Delta R$  (tolerance).

Let  $\Delta R_L / R_L = 2p$  (value not %).

If  $R_L \gg \Delta R_L$  then  $CMRR = 20 \log \left( \left( \frac{1}{2p} \right) \left( \frac{R_L}{R_S} \right) \right) \text{ dB}$

a) S9;  $R_{in(DM)} = 2R_1 = 2(4.7\text{k}) = 9.4 \text{ k}\Omega$

b) S9;  $A_{DM} = \frac{-R_2}{R_1} = \frac{-270}{4.7} = -57.45$

c) S9;  $R_{in(CM)} = \frac{2R_1 + 4.7}{2} = 137.35 \text{ k}\Omega$


d) S10;  $A_{CM} = \frac{V_{out}}{V_{in}} = \frac{\Delta R_2}{R_2} (A_{DM}) = \frac{\Delta R_2}{R_1} = \frac{(2p)(R_2)}{R_1} = \frac{270(2)(0.01)}{4.7} = 1.15$

e) S11; CMRR can be found by substituting  $V_{in}$  for  $V_{DM}$  giving


$$CMRR = 20 \log \left( \frac{V_{DM}}{V_{CM}} \right) = 20 \log \left( \frac{R_2}{\Delta R_2} \right) = 20 \log \left( \frac{1}{2p} \right) \text{ dB} = 20 \log \left[ \frac{1}{2(0.01)} \right] = 33.98 \text{ dB}$$

Q3


Part A

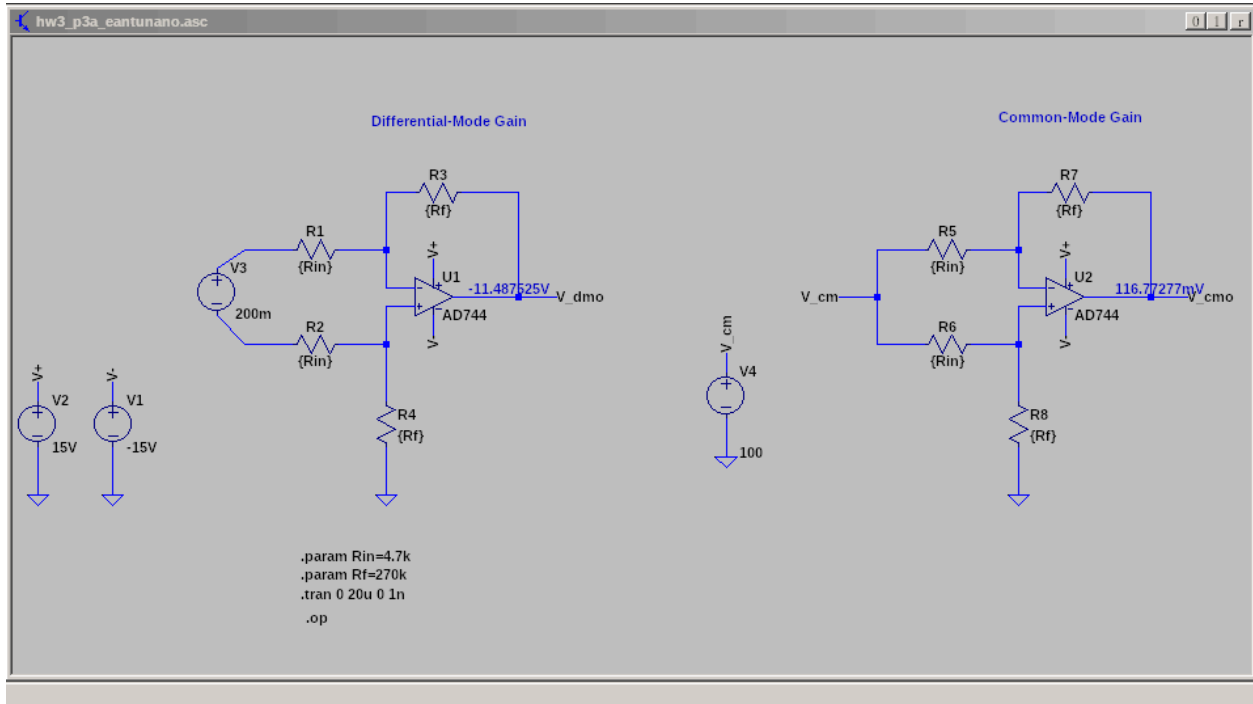


Part B 5V

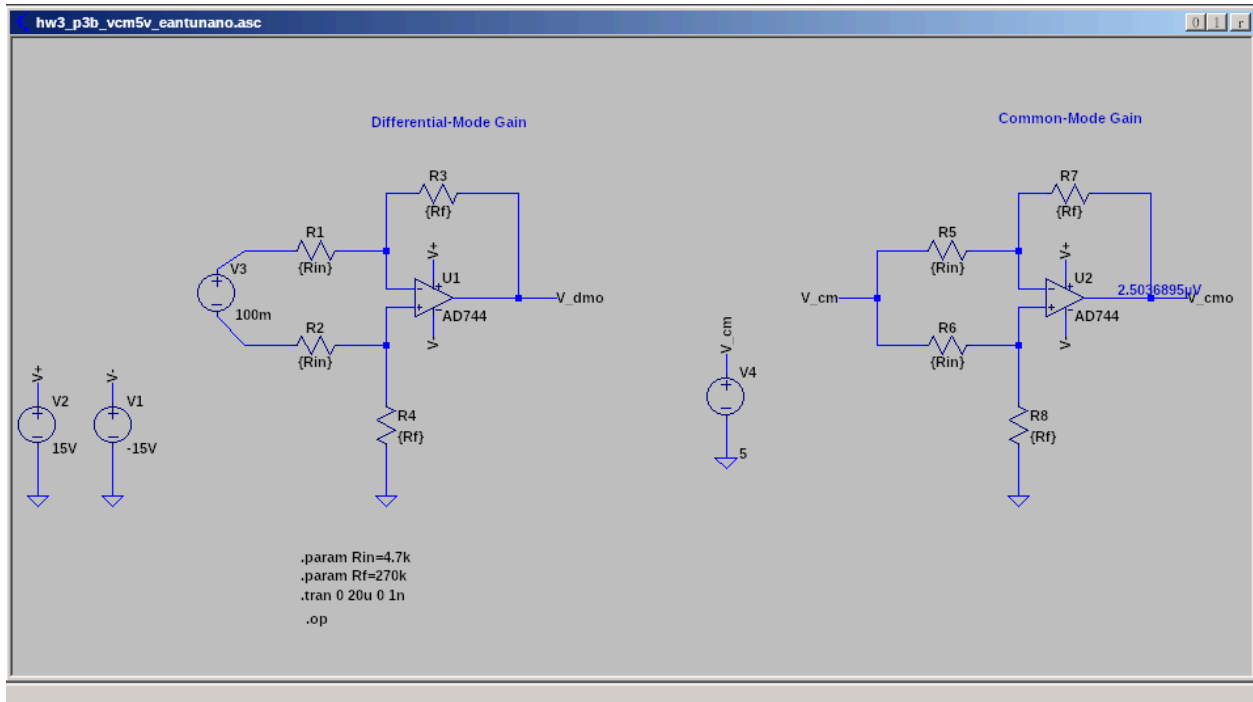


## Part B 10V

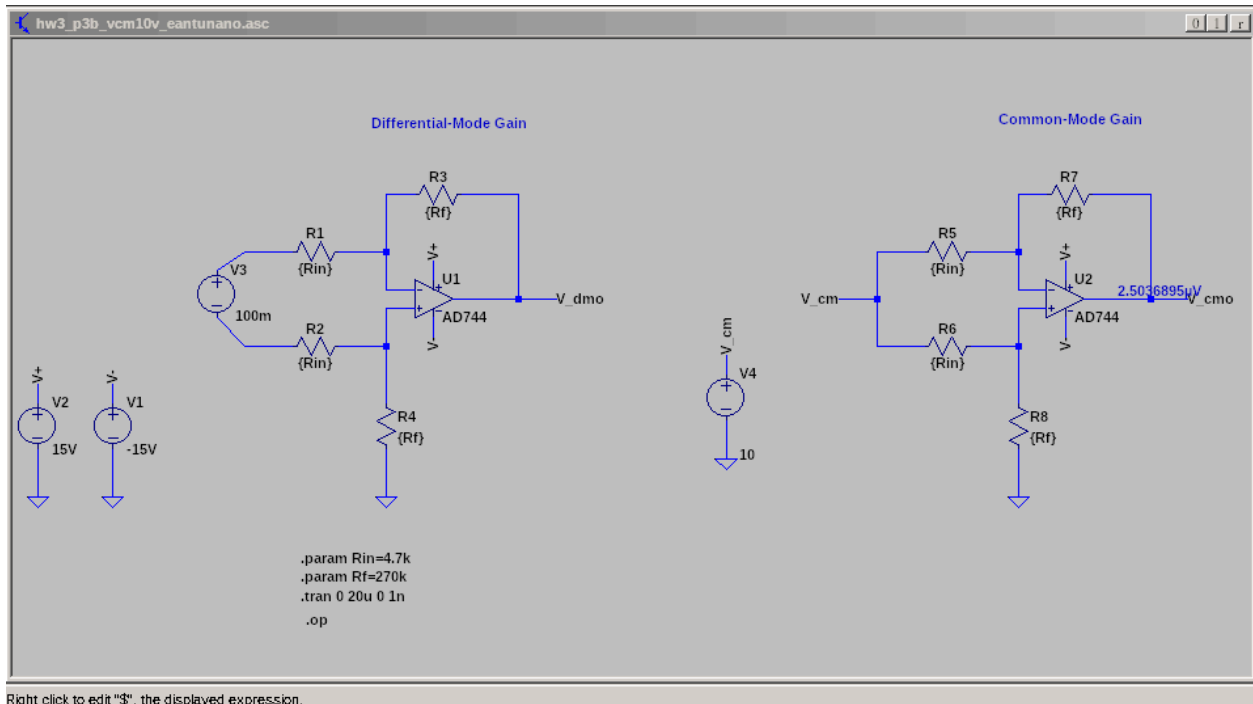

## Part C 5V

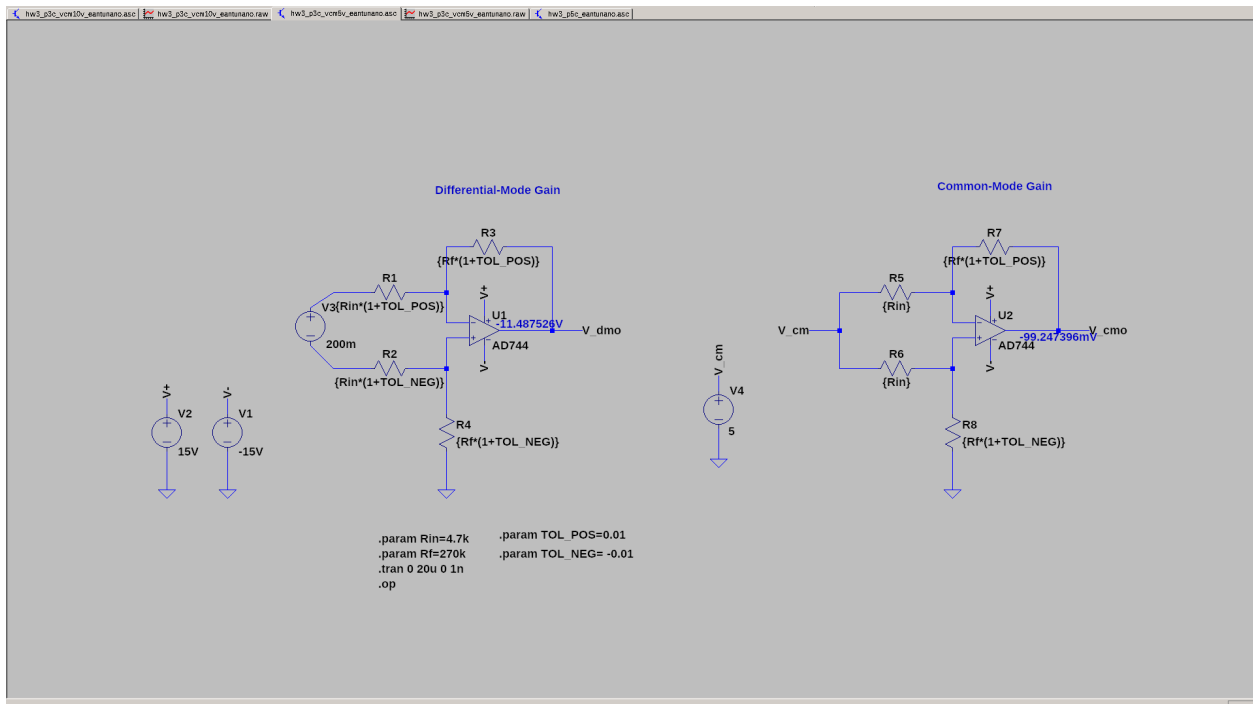

## Part C 10V

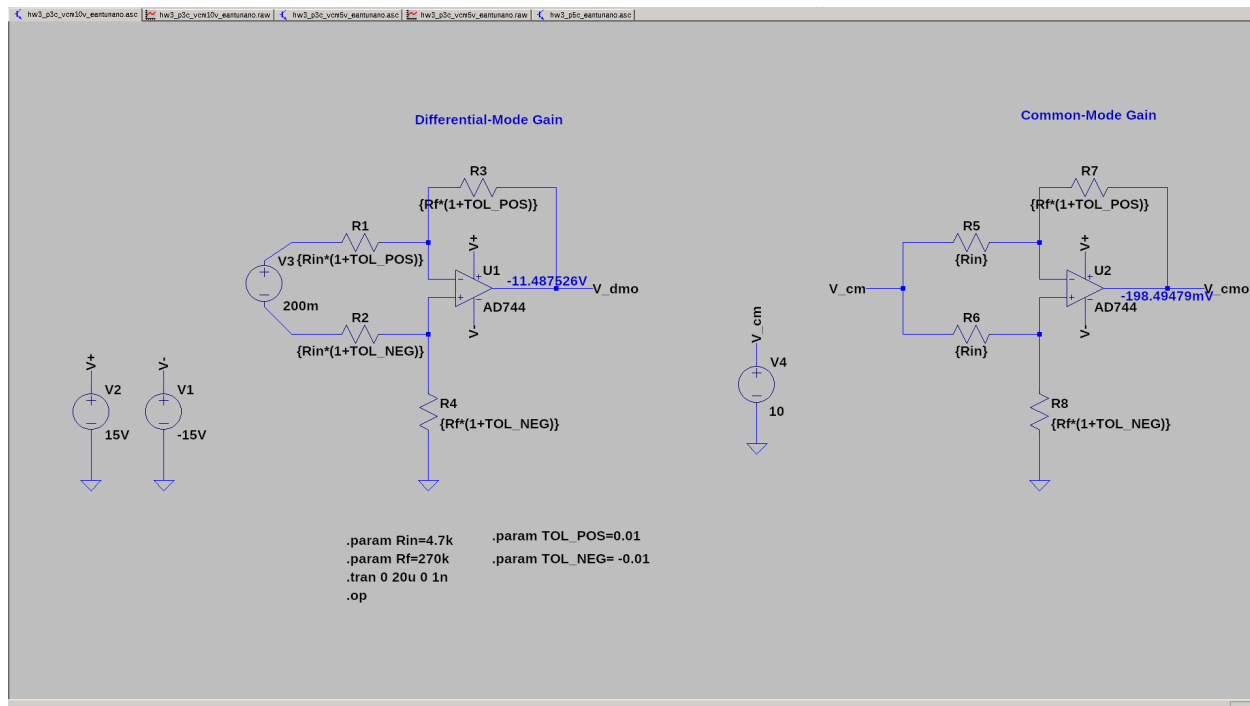

**Q3 [7 pts]:** In LTSPICE, build the circuit shown in Figure 1 (using an AD744 op-amp) with the values of  $R1$  and  $R2$  as specified by the question.

- Find the DM gain and the CM gain via the application of  $V_{DM}=0.2$  and  $V_{CM}=100$ .
- Using the application note attached for CMRR calculation in simulation models (on moodle), Find the idea CMRR of the circuit in part (a) (use  $\Delta V_{in}=5V$ , i.e. one case 10V the other 5V).
- Apply a resistor tolerance of 1% such that you ADD 1% to  $R2$  values and you subtract 1% from  $R1$  values. Simulate and calculate the CMRR value obtained from your simulation model (again using the method in the application note provided on moodle).
- Explain the results your obtained in (b) and (c) with respect to the ideal calculation.

[Hint: Check the data sheet of the amplifier to know some of its features as well as its biasing levels]

$$S11: CMRR = 20 \log \left( \frac{V_{cm}}{V_{dm}} \right) = 20 \log \left( \frac{R_2}{2R_1} \right) = 20 \log \left( \frac{1}{2} \right) dB$$

$$a) A_{dm} = \left| \frac{V_o}{V_{in}} \right| = \left| \frac{-11.49}{0.2} \right| = 57.45 \quad A_{cm} = \left| \frac{V_o}{V_{in}} \right| = \left| \frac{0.117}{100} \right| = 0.00117$$

From app. note:

$$b) CMRR = \frac{\Delta V_{in}}{\Delta V_{out}} \left( 1 + \frac{R_2}{R_1} \right) = 20 \log \left( \frac{10V - 5V}{2.5\mu V - 1.25\mu V} \left( 1 + \frac{270K}{4.7K} \right) \right)$$

$$= 167.38 \text{ dB}$$

$$c) CMRR = \frac{\Delta V_{in}}{\Delta V_{out}} \left( 1 + \frac{R_2}{R_1} \right) = 20 \log \left( \frac{10V - 5V}{178.49\mu V - 91.25\mu V} \left( 1 + \frac{270K(1+0.01)}{4.7K(1+0.01)} \right) \right) = 69.38 \text{ dB}$$

- d) The CMRR dips significantly in part c because the variation in resistors  $R_f$  cause the  $A_{cm}$  to increase. In part b), the ideal case,  $A_{cm}$  is kept as close to zero as possible, which following  $20 \log (V_{cm}/V_{dm})$  dB keeps a high CMRR. With tolerance, a larger  $A_{cm}$  decreases the CMRR since  $A_{dm}$  remains constant even if  $R_f$  changes.

## Q4

**Q4 [10 pts]:** A large microprocessor draws a total transient current of 10A from a 3.3V supply. The logic has a rise/fall time of 1ns. It is desirable to limit the Vcc to ground noise voltage peaks to 250mV, and each decoupling capacitor has 5nH of series inductance. The decoupling will be done with a multiplicity of equal value capacitors and should be effective at all frequencies above 20MHz.

- Sketch the value of the target impedance versus frequency
- What is the minimum number of decoupling capacitors required to fulfil the requirements?
- What should be the minimum value of each of these capacitors?

(d) Could larger value capacitors be used just as effectively? S30; increasing the value of the overall capacitance can decrease the overall impedance, which is the recommended technique

Question:

S32; for the target impedance would the anti-resonance spikes be acceptable if they exceeded the target impedance even if the resonance dips were under the target impedance curve?


a) S33; example solution

Assume correction factor  $k=2$

$$Z_t = k \left( \frac{dV}{dI} \right)$$

$$Z_t = (2) \left( \frac{330 \times 10^{-3}}{10} \right) = 0.05 \Omega = 50 \text{ m}\Omega$$
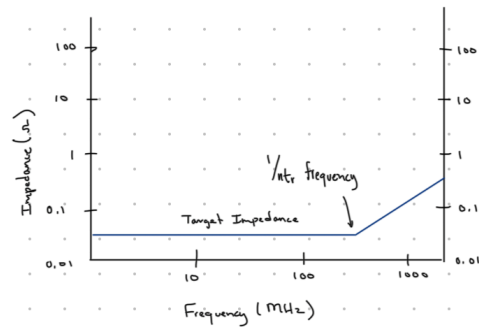
$$\text{corner frequency: } \frac{1}{\pi \tau_r} = \frac{1}{\pi (1 \times 10^{-9})} = 318 \text{ MHz}$$



b) S32, minimum number of caps (n) to achieve a certain target impedance

$$n = \frac{2L}{Z_t \tau_r} \text{ where the inductance } L \text{ is the total inductance (caps, traces, IC, leads)}$$

$Z_t$  = target impedance

$\tau_r$  = rise time

$$n = \frac{2(5 \times 10^{-9})}{(50 \text{ m})(1 \times 10^{-9})} = 200 \text{ caps}$$

c) S33; example solution

$$Z_c = \frac{1}{\omega C} \rightarrow C = \frac{1}{\omega Z_c}$$

$Z_c$  = target impedance

$\omega$  = lowest freq of interest

$C$  = total capacitance

$$C = \frac{1}{(20 \times 10^6)(50 \times 10^{-3})2\pi} = 159 \text{ nF}$$

$$\frac{C}{n} = \frac{159 \text{ nF}}{200} = 795 \text{ pF per cap}$$

d) Purely for this problem, higher value caps would be effective. The only drawback is that the resonance frequency's overall impedance would reach a minimum at a lower frequency with fewer large caps and a constant overall capacitance. The signal's rise/fall time would be lower.



Q5

S13;

Instead of using  $R_2$ , two buffer amplifiers can be added to the inputs of a standard amplifier to improve CMRR.

The benefit of the amplifier is that there's a single resistor value for gain control ( $kR_F$ )

Output voltage for amplifier  $V_o = (V_2 - V_1) \left( 1 + \frac{2R_F}{kR_F} \right) \left( \frac{R_1}{R_1} \right)$

$$\text{CMRR: } 20 \log \left( \frac{A_{dm}}{A_{cm}} \right) = 20 \log \left( \frac{A_{dm}}{2p} \right) = 20 \log \left( \frac{1 + \frac{2}{k}}{2p} \right) \text{ dB}$$

For the same tolerance resistors in a differential amp, an instrumentation one will provide a CMRR that is  $20 \log(A_{dm})$  higher.

a)  $A_{DC} = \frac{V_o}{V_2 - V_1} = \left( 1 + \frac{2(100)}{100} \right) = 1 + 20 = 21$

b) S13;

$$100 = k(1000) \\ k = 0.1$$

$$\text{CMRR} = 20 \log \left( \frac{1 + \frac{2}{k}}{2p} \right) = 20 \log \left( \frac{1 + \frac{2}{0.1}}{2(0.01)} \right) =$$

$$\boxed{\text{CMRR} = 60.42 \text{ dB}}$$

c)  $A_{dm} = \frac{V_o}{V_i} = \left| \frac{-4.16 \text{ V}}{200 \text{ mV}} \right| = 20.8$


$$\text{CMRR} = \frac{\Delta V_{in}}{\Delta V_{out}} \left( 1 + \frac{R_2}{R_1} \right) = 20 \log \left( \frac{10 \text{ V} - 5 \text{ V}}{(148.56 - 490.74) \text{ V}} \left( 1 + \frac{10 \text{ k} (1 + 0.01)}{10 \text{ k} (1 - 0.01)} \right) \right) = 146.87 \text{ dB}$$

Is it  $\frac{R_1(+\%) }{R_1(-\%)}$  for an instrumentation amplifier?


Spice model  $V_{cm} = 0$

d) -3dB point @ 649.49 kHz for  $A_{dm}$   
3dB point @ 23.667 Hz for  $A_{cm}$

## Part C 5V

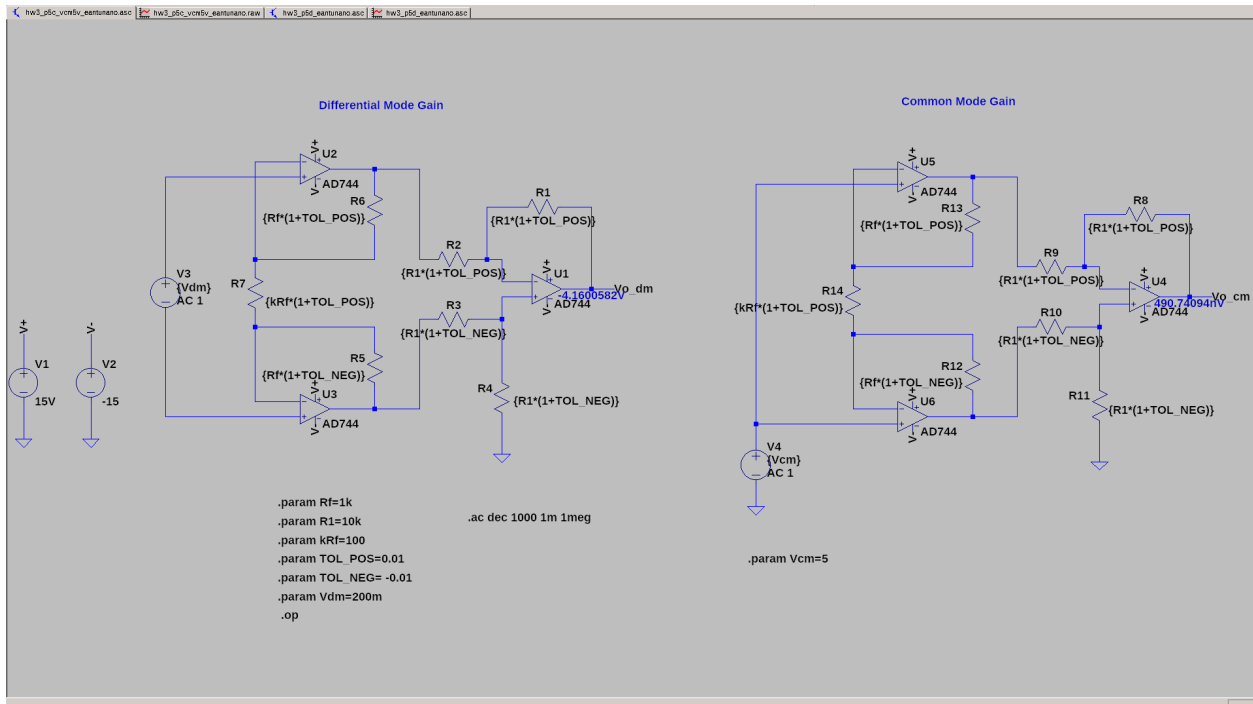

## Part C 10V

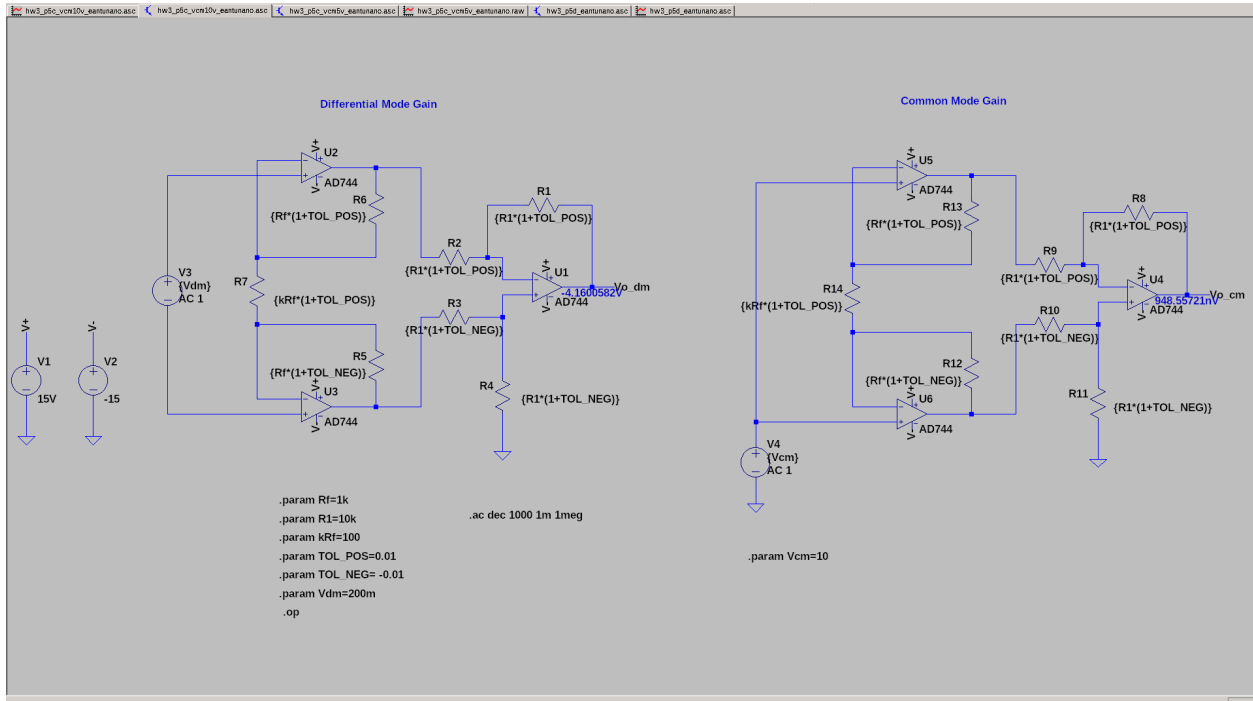

## Part D

